 


● Gate-Level Testing. Detection of SSF's

Test Tables

Example 1: AND gate  $y = f(x_1, x_2)$



$x_1$	$x_2$	$f(x_1, x_2)$	$\hat{f}(x_1, x_2)$					
			$x_1/0$	$x_1/1$	$x_2/0$	$x_2/1$	$y/0$	$y/1$
0	0	0	0	0	0	0	0	1
0	1	0	0	1	0	0	0	1
1	0	0	0	0	0	1	0	1
1	1	1	0	1	0	1	0	1

Test Table:

$x_1$	$x_2$	$x_1/0$	$x_1/1$	$x_2/0$	$x_2/1$	$y/0$	$y/1$
0	0	0	0	0	0	0	1
0	1	0	1	0	0	0	1
1	0	0	0	0	1	0	1
1	1	1	0	1	0	1	0

● Optimal test  $T = \{01, 10, 11\}$  in every  
column at least one 1

$x_1/0$   $x_2/0$   $y/0$  have the same column  $\Rightarrow$  cannot be located

Example 2

OR gate



Test table:

$x_1$	$x_2$	$x_1/0$	$x_1/1$	$x_2/0$	$x_2/1$	$y/0$	$y/1$
0	0	0	1	0	1	0	1
0	1	0	0	1	0	1	0
1	0	1	0	0	0	1	0
1	1	0	0	0	0	1	0

Optimal test:  $T = \{00, 01, 10\}$

For  $m$ -input AND gate:  $T = \{11...11, 01...11, \dots, 11...10\}$

For  $m$ -input OR gate:  $T = \{00...00, 10...00, \dots, 00...01\}$

Testing of  $m$ -input AND OR gates:  $|T| = m$   
(Linear test complexity)

Example 3

XOR gate



Test Table:

$x_1$	$x_2$	$x_1/0$	$x_1/1$	$x_2/0$	$x_2/1$	$y/0$	$y/1$
0	0	0	1	0	1	0	1
0	1	0	1	1	0	1	0
1	0	1	0	0	1	1	0
1	1	1	0	1	0	0	1

Test :  $T = \{00, 01, 11\}$


For  $M$  input XOR gate  $T = \{00\dots 0, 11\dots 1, 00\dots 01\}$

The number of test patterns  $|T| = 3$  does not depend on a number of inputs  $M$ .

# Testing Internal Faults -

-Dependence on an implementation


Example - parity checkers

 

$x_1 \oplus x_2 \oplus x_3 \oplus x_4 \Rightarrow$  3 test patterns:

0000  
1101  
0111

0010  
1111  
0011  
0100

 

$x_1 \oplus x_2 \oplus x_3 \oplus x_4 \Rightarrow$

9 test patterns:

0001  
0010  
0100  
1000  
1110  
1101  
1011  
0111  
0000

For a m-bit binary tree

$$y = x_1 + x_2 + \dots + x_m$$

And single stuck-at faults

<b>IMPLEMENTATION</b>	<b>Min. # of test patterns</b>
Tree of XOR Gates	3
Two-Level AND-OR Network	$2^{m-1} + 1$

## Generation of a Minimal Test

choose a minimal number of rows in the test table containing at least one 1 in every column

Covering problem  $\Rightarrow$  NP-complete

Good practical solutions for small networks by branch and bounds method

Diagnostic (Fault Location) for  
Combinational Networks

Even more difficult than fault de-  
tection - mostly for manufacturing  
(not a field) test

Test table:  $(t_{ij}) = 1$  iff test pattern  $t_i$   
detects  $j$ th faults

Fault Detection: min number of rows  
such that every column  
contains at least one 1

Fault Location min number of different  
nonzero columns

Lower Bounds for a number of  
Test Patterns for Location of  
Stuck-at Faults

$$|T| \geq \lceil \log_2 \sum_{i=0}^L 2^i \binom{L}{i} \rceil$$

$|T|$  is a number of test patt


$L$  is a number of lines

$l$  is a multiplicity of fault

Example  $L=1,000$  ,  $l=2 \Rightarrow |T| \geq 2$



# PATH SENSITIZATION

 

1. SPECIFY INPUTS  $x_i$  TO PRODUCE FAULTY CONDITION  $A=B=1$


2. SELECT PATH FROM FAULT TO PO (ERROR PROPAGATION)  $R-G_3-Z$

3. SENSITIZE PATH FROM FAULT TO PO (LINE JUSTIFICATION)  $S=0 \Rightarrow C=D=1$


Test pattern  $ABCD = (1111)$

ERROR PROPAGATION



$x \rightarrow z$

 


$\Rightarrow x_2 = x_3 = 1$

 

$\Rightarrow x_2 = x_3 = 0$

  

$\Rightarrow x_2 = *$

 

Consider: a s-a-0 a/o

1. PROVOKE FAULT

2. PROPAGATE "FAULT EFFECT"

3. LINE JUSTIFICATION

PATH SENSITIZATION

1.  $A \cdot B \cdot C = 0 \Rightarrow A=0 \text{ or } B=0 \text{ or } C=0$

2. Path a - G6 - z2

3.  $b=1 \Rightarrow E=d=0 \Rightarrow C=1$

test patterns:

	A	B	C	E	E
	0	*	1	0	*
	*	0	1	0	*

$0 * 1 0 * =$

00100
01100
00101
01101

$* 0 1 0 * =$

00100
00101
10100
10101

## Gate-level Testing. Conclusions

10.7

1. SSF model is the most popular
2. Gate-level testing is very complicate even for SSF for VLSI. (test generation time  $\sim 2^N$  in the worst case and  $\sim N^3$  on average)
3. Most existing algorithms cannot generate a (even not optimal!) test for  $N > 2 \cdot 10^4$
4. For complex devices ( $\mu$ processors) fault-coverage of (95-96)% is sufficient for practical purposes
5. Simulation to estimate fault-coverages. Software for simulation expensive. Simulation is slow. (About 50 hours for a chip with  $N = 10^5$ )
6. Very difficult to generate a test for sequential networks