

## Relationship between

TESTING AND DESIGN

VERIFICATION

DESIGN VERIFICATION IS FOR  
man-made design errors

TESTING IS FOR physical defects

- FOR physical defects (faults)  
one can develop fault models  
Then faults can be enumerated  
and the quality of a test  
can be estimate by the  
fault coverage

- FOR design errors the space of errors is not enumerable in most cases.

It is difficult to estimate a quality of a design verification procedure

Typical design errors are related to the sequencing of the data transfers and transformations rather than to the data operations, since DATA OPERATIONS ARE "LOCAL".

Most design verification procedures  
are based on SIMULATION

### PROBLEMS:

1. Generation of input patterns
2. Estimation of results of verification (correctness of the design)
3. Estimation of completeness of test.
4. Simulation time.

A system which passes the design verification is shown to be correct only with respect to the test applied

Completeness of the test cannot be rigorously determined.

TEST GENERATION FOR DESIGN VERIFICATION is generally a heuristic process

FOR LSI/VLSI devices DESIGN VERIFICATION is very IMPORTANT  
(high cost of design error)

HIERARCHICAL DESIGN VERIFICATION:



1. HIGHEST-LEVEL FORMAL MODEL (e.g. RTL model) is checked against the INITIAL INFORMAL model

2. HIGHER-LEVEL MODEL defines a specification for its implementation at the lower level

3. Checking the lower level implementation is reduced to verification of this specification. This can be obtained by applying the same tests to the higher and lower level models; and the results from the higher-level model are expected results for the lower-level model.

(Sasaki et al. "Hierarchical design verification for large digital systems", Proc. 18th Design Automation Conf. pp105-112, 1981)

# TRANSISTORS

 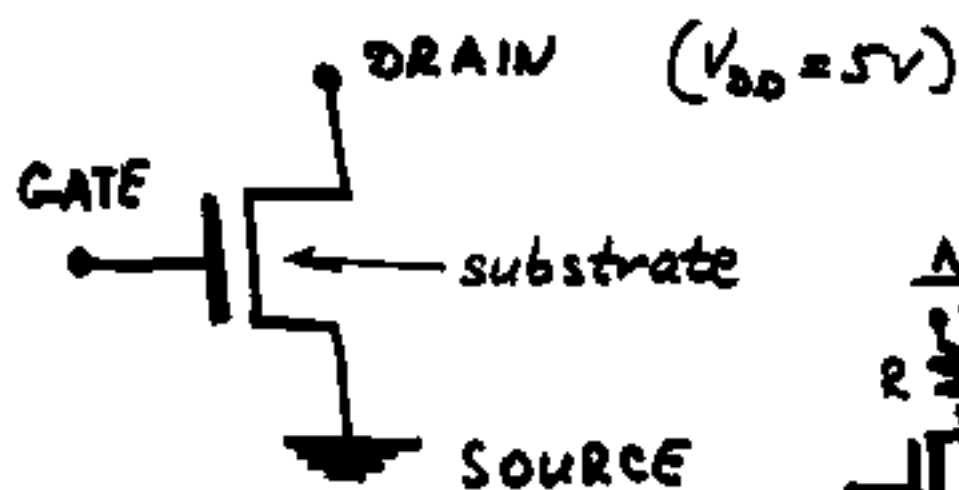

1. CLOSED SWITCH (OFF)

VOLTAGE AT GATE 0

NO CURRENT FROM  $V_{DD}$  through  $R$ .  
HIGH VOLTAGE AT OUTPUT

2. OPEN SWITCH (ON)

INPUT VOLTAGE AT GATE  $V_{DD}$

CURRENT FROM  $V_{DD}$  through  $R$ .


LOW VOLTAGE AT OUTPUT

N. Jha, S. Kundu "Testing and Reliable  
DESIGN OF CMOS CIRCUITS"

KLUWER PUBLISHERS, 1990

# CMOS TRANSISTOR LOGIC (STATIC)

## COMPLEMENTARY LOGIC

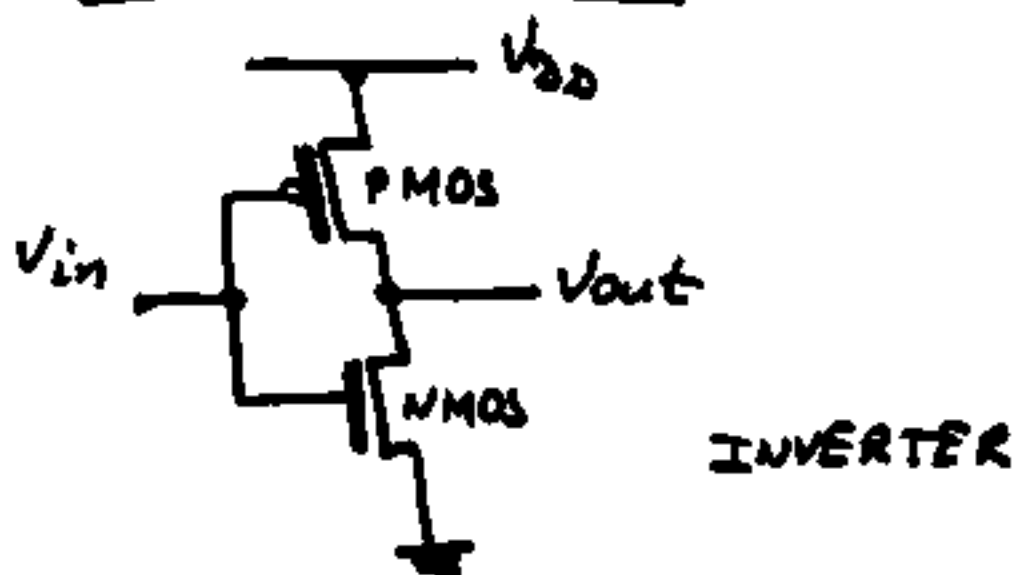

If  $V_{in}$  high

NMOS CONDUCTS

PMOS NONCONDUCTIVE

$V_{out}$  low

$$V_{out} = \overline{V_{in}}$$

If  $V_{in}$  LOW

NMOS NON CONDUCTIVE

PMOS CONDUCTIVE

$V_{out}$  high.


## CMOS LOGIC

Advantages for high density chips:


- LOW POWER CONSUMPTION
- HIGH NOISE IMMUNITY  
(MAX NOISE VOLTAGE WHICH CAN BE TOLERATED)
- ONLY one transistor conducts at any time.  
Little current from  $V_{DD}$  to ground. Low heat dissipation  
Most faults results in THE DRASTIC INCREASE OF THIS CURRENT (IDDQ TEST)
- both transistors ARE PARTIALLY ON DURING THE SWITCHING OPERATION



# CMOS NAND (STATIC)

 


# CMOS NOR

 

# DYNAMIC CMOS (DOMINO)

## EXAMPLE

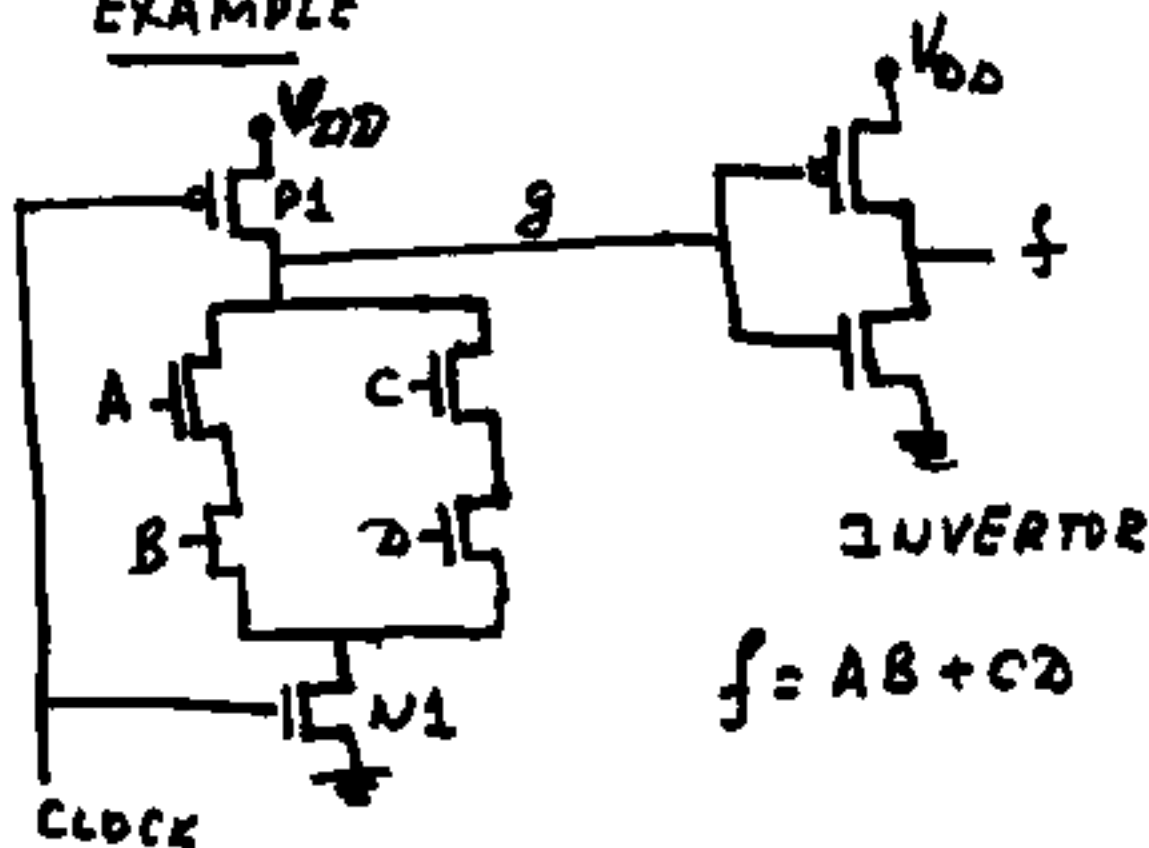

If  $CLOCK = 0$   $P1$  conducts  
and precharge  $g \Rightarrow f = 0$   
(precharge phase)

If  $CLOCK = 1$   $N1$  conducts  
(evaluation phase)  $\Rightarrow$

$$f = AB + CD$$

• EVERY COMPLEX<sup>-76</sup> GATE IS FOLLOWED  
by INVERTER

• Outputs of invertors = 0 during  
precharge phase.

• primary inputs (A, B, C, D)  
are changed only during  
precharge phase.

• DOMINO CMOS requires  
less area on the chip than  
STATIC CMOS.

• DOMINO may require more  
power than static (for  
precharging)

• DOMINO IS FULLY COMPATIBLE  
WITH STATIC CMOS