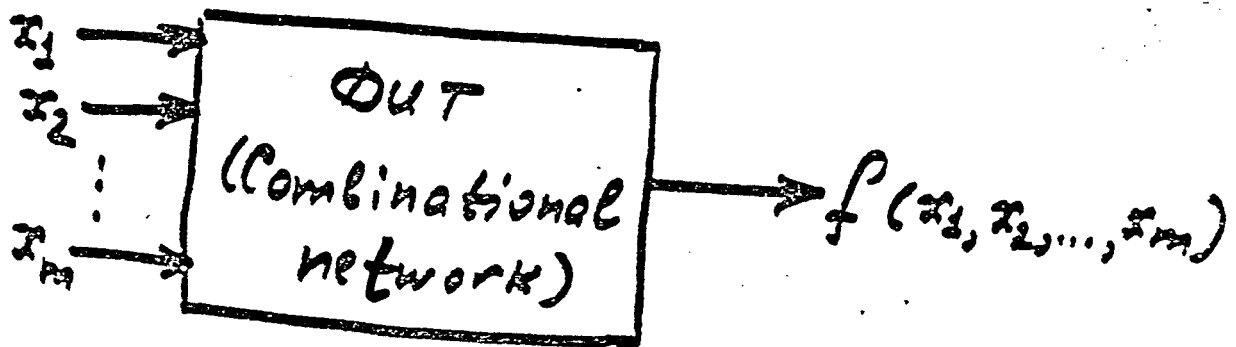


Boolean Differences

(Boolean derivatives)

Efficient analytical technique
for test generation for SFS

Problem: for a given fault construct
all test patterns detecting



Definition:

$$\frac{\partial f}{\partial x_1}(x_2, \dots, x_m) = f(0, x_2, \dots, x_m) \oplus f(1, x_2, \dots, x_m)$$

Testing by Boolean Difference

Theorem: (i) Input pattern (t_2, \dots, t_m) detects

$x_i/0$ iff

$$t_1 \frac{\partial f}{\partial x_i}(t_2, \dots, t_m) = 1$$

(ii) (t_2, \dots, t_m) detects $x_i/1$

iff

$$\bar{t}_1 \frac{\partial f}{\partial x_i}(t_2, \dots, t_m) = 1$$


Test generation for detection of $x_i/0$
and $x_i/1$ reduces to computation

of $\frac{\partial f}{\partial x_i}$

(3) $x_i/0$ and $x_i/1$ are undetectable iff

$$\frac{\partial f}{\partial x_i} = 0$$

Example 1

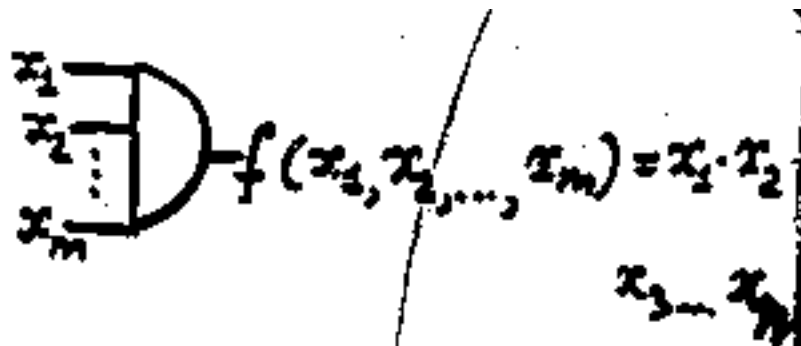


$$\frac{\partial f}{\partial x_1} = 0 \cdot x_2 \cdot \dots \cdot x_m \oplus 1 \cdot x_2 \cdot \dots \cdot x_m = x_2 \cdot x_3 \cdot \dots \cdot x_m$$

Fault	Condition for test	test pattern
$x_1/0$	$x_1 x_2 x_3 \dots x_m = 1$	1 1 1 ... 1
$x_1/1$	$\bar{x}_1 x_2 x_3 \dots x_m = 1$	0 1 1 ... 1
$x_2/0$	$x_1 \bar{x}_2 x_3 \dots x_m = 1$	1 0 1 ... 1
$x_2/1$	$x_1 x_2 \bar{x}_3 \dots x_m = 1$	1 1 0 ... 1
\vdots		
$x_m/0$	$x_1 x_2 x_3 \dots \bar{x}_m = 1$	1 1 1 ... 0
$x_m/1$	$x_1 x_2 x_3 \dots x_m = 1$	1 1 1 ... 1

Optimal test:

0 1 1 ... 1 1	} $m+1$ test pattern.
1 0 1 ... 1 1	
1 1 0 ... 1 1	
...	
1 1 1 ... 0 1	
1 1 1 ... 1 0	
1 1 1 ... 1 1	

Example 2

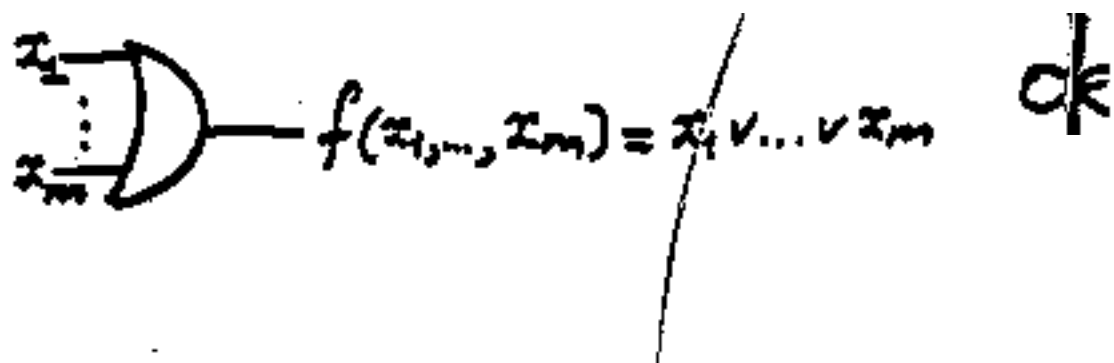

$$\frac{\partial f}{\partial x_i} = (x_1 \vee \dots \vee x_{i-1} \vee 0 \vee x_{i+1} \vee \dots \vee x_m) \oplus$$

$$(x_1 \vee \dots \vee x_{i-1} \vee 1 \vee x_{i+1} \vee \dots \vee x_m) =$$

$$= (x_1 \vee \dots \vee x_{i-1} \vee x_{i+1} \vee \dots \vee x_m) \oplus 1 =$$


$$= \bar{x}_1 \dots \bar{x}_{i-1} \bar{x}_{i+1} \dots \bar{x}_m$$

Optimal test:

$$\left. \begin{array}{cccc} 1 & 0 & \dots & 00 \\ 0 & 1 & \dots & 00 \\ \dots & \dots & \dots & \dots \\ 00 & \dots & 1 & 0 \\ 00 & \dots & 0 & 1 \\ 00 & \dots & 0 & 0 \end{array} \right\}$$

$m+1$ test patterns

Example 3

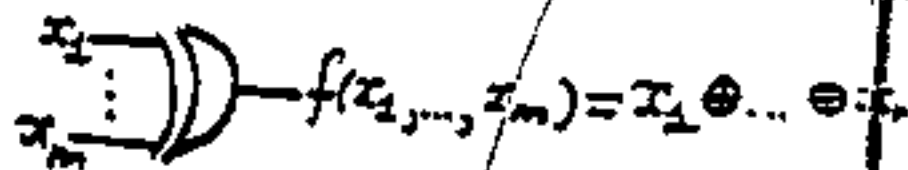

$$\frac{\partial f}{\partial x_i} = (x_1 \oplus \dots \oplus x_{i-1} \oplus 0 \oplus x_{i+1} \oplus \dots \oplus x_m) \oplus$$

$$(x_1 \oplus \dots \oplus x_{i-1} \oplus 1 \oplus x_{i+1} \oplus \dots \oplus x_m) = 1$$

Optimal test

$$\begin{array}{c} 00 \dots 00 \\ 11 \dots 11 \end{array}$$

detects all single input stuck-at faults
for any m

XOR gates have better testability than
AND and OR gates

Properties of Boolean Differences

Rules of Algebraic Manipulations for computing $\frac{\partial f}{\partial x_i}$


1. NOT $\frac{\partial f}{\partial x_i} = \frac{\partial f}{\partial x_i}$ (e.g. $\frac{\partial (f \vee g)}{\partial x_i} = \frac{\partial (f \bar{g})}{\partial x_i}$)

2. AND $\frac{\partial (f \cdot g)}{\partial x_i} = f \frac{\partial g}{\partial x_i} \oplus g \frac{\partial f}{\partial x_i} \oplus \frac{\partial f}{\partial x_i} \frac{\partial g}{\partial x_i}$

3. OR $\frac{\partial (f \vee g)}{\partial x_i} = \bar{f} \frac{\partial g}{\partial x_i} \oplus g \frac{\partial f}{\partial x_i} \oplus \frac{\partial f}{\partial x_i} \frac{\partial g}{\partial x_i}$

4. XOR $\frac{\partial (f \oplus g)}{\partial x_i} = \frac{\partial f}{\partial x_i} \oplus \frac{\partial g}{\partial x_i}$


5. Simple Chain Rule

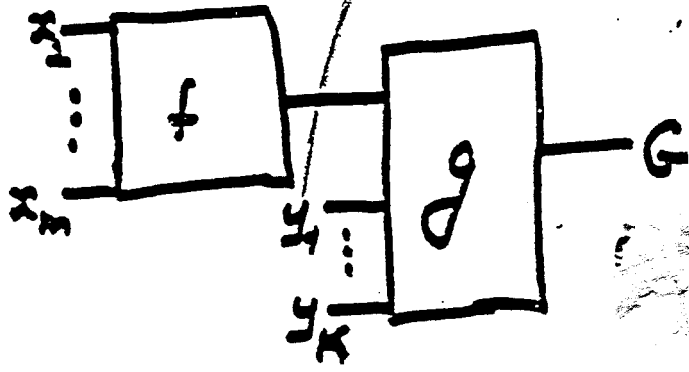

$$x_i \neq y_j$$

$$\frac{\partial G}{\partial x_i} = \frac{\partial g}{\partial f} \cdot \frac{\partial f}{\partial x_i}$$

Example

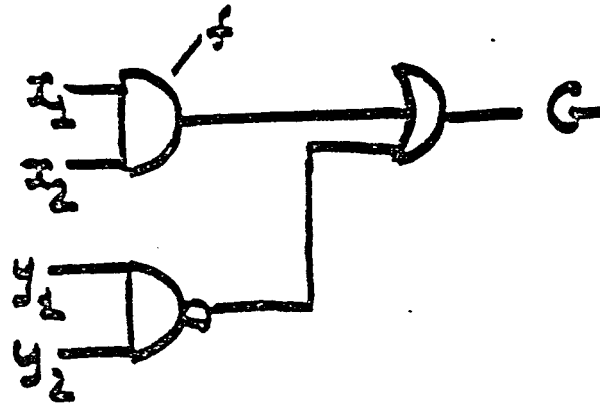

$$f = x_1 x_2$$

$$g = f \vee \overline{y_1 y_2}$$

$$\frac{\partial g}{\partial f} = \overline{y_1 y_2} \oplus 1 = y_1 y_2, \quad \frac{\partial f}{\partial x_2} = x_1 \Rightarrow$$


$$\frac{\partial G}{\partial x_2} = y_1 y_2 x_1$$

x1/0
x1/1

x1	x2	
1	1	1
1	0	1
0	1	1
0	0	1
	y1	y2

Example

MAJORITY GATE

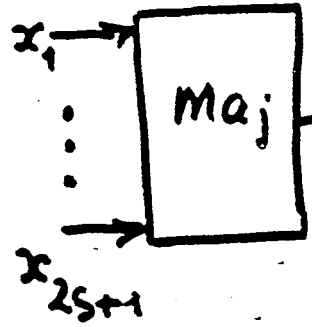

$$f(x_1, \dots, x_{2s+1}) = \begin{cases} 1, & \sum_{i=1}^{2s+1} x_i \geq s+1 \\ 0, & \sum_{i=1}^{2s+1} x_i < s+1 \end{cases}$$

Let $T_r(m) = T_r(x_1, \dots, x_m) = \begin{cases} 1, & \sum_{i=1}^m x_i \geq r \\ 0, & \sum_{i=1}^m x_i < r \end{cases}$

$$\text{Maj}(x_1, \dots, x_{2s+1}) = T_{s+1}(2s+1)$$

$$\frac{\partial \text{Maj}}{\partial x_1} = \text{Maj}(0, x_2, \dots, x_{2s+1}) \oplus$$

$$\text{Maj}(1, x_2, \dots, x_{2s+1}) =$$

$$= T_{s+1}(x_2, \dots, x_{2s+1}) \oplus T_s(x_2, \dots,$$

$$= T_{s+1}(2s) \oplus T_s(2s) \Rightarrow x_{2s+1}$$

$$\frac{\partial \text{Maj}}{\partial x_1} = 1 \Leftrightarrow \sum_{i=2}^{2s+1} x_i = s$$

$$\frac{\partial \max_j}{\partial x_i} = 1 \iff \sum_{j \neq i} x_j = s$$

Test patterns:

$$\underbrace{0 \ 0 \ \dots \ 0}_s \ \underbrace{1 \ 1 \ \dots \ 1}_{s+1}$$

$$\underbrace{1 \ 1 \ \dots \ 1}_{s+1} \ \underbrace{0 \ 0 \ \dots \ 0}_s$$

$$\underbrace{0 \ 0 \ \dots \ 0 \ 0}_{s+1} \ \underbrace{1 \ 1 \ \dots \ 1}_s$$

$$\underbrace{1 \ 1 \ \dots \ 1}_s \ \underbrace{0 \ 0 \ 0 \ \dots \ 0}_{s+1}$$

Faults detected

$$x_i / 0 \quad i = s+1, \dots, 2s+1$$

$$x_i / 0 \quad i = 1, \dots, s$$

$$x_i / 1 \quad i = 1, \dots, s$$


$$x_i / 1 \quad i = s+1, \dots, 2s+1$$

Constant Test Complexity

4 test patterns for any $n = 2s+1$

Example 4

DATA

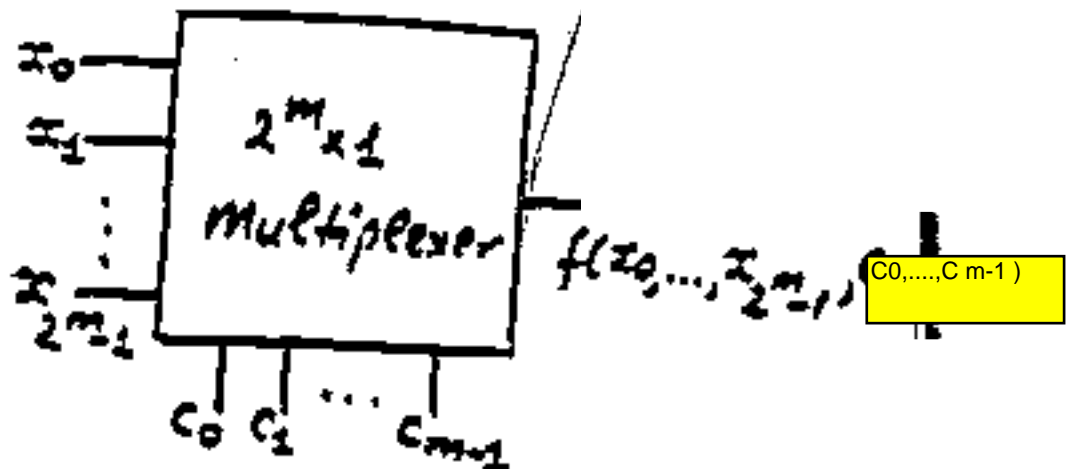

$f = x_i$ if $c = i$ CONTROL

$$\frac{\partial f}{\partial x_0} = \begin{cases} 1, & c = (0, 0, \dots, 0); \\ 0, & \text{otherwise} \end{cases};$$

$$\frac{\partial f}{\partial x_i} = \begin{cases} 1, & c = (c_0, \dots, c_{m-1}) = i; \\ 0, & c \neq i \end{cases};$$

Optimal test:

$2 \cdot 2^m$ test

patterns


detects all

I/O SFS.

	x_0	x_1	...	x_{2^m-1}	c_0	c_1	...	c_{m-1}	
}	0	0	...	0	0	0	...	0	$x_0/1$
	1	0	...	0	0	0	...	0	$x_0/0, c_0$
	0	0	...	0	0	0	...	1	$x_1/1$
	0	1	...	0	0	0	...	1	$x_1/0$

	0	0	...	0	1	1	...	1	$x_{2^m-1}/1$
	0	0	...	1	1	1	...	1	$x_{2^m-1}/0$
									$c_i/0$

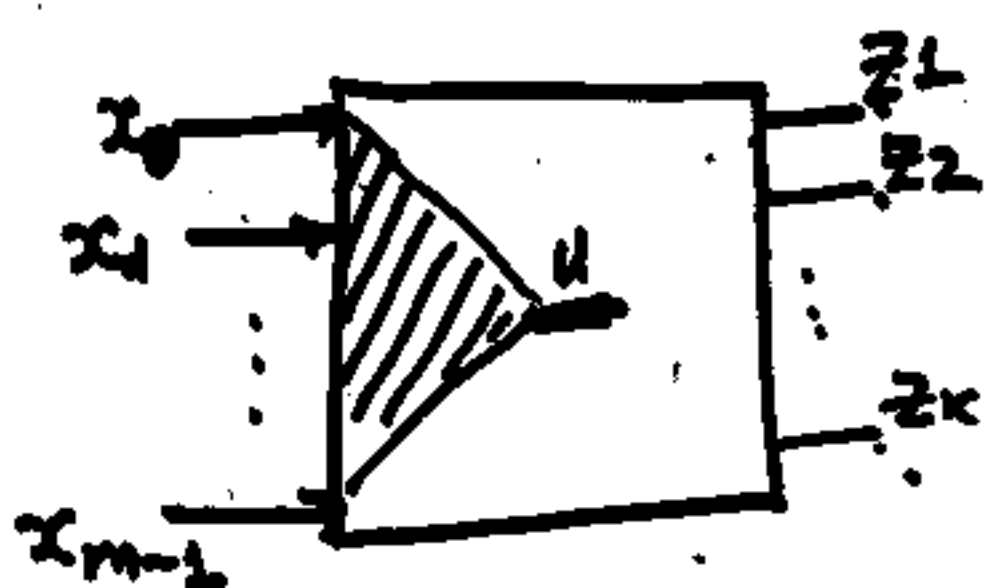DETECTION OF STUCK-AT FAULTS
(SSFS) AT INTERNAL LINES
FOR DEVICES WITH MULTIPLE
OUTPUTS by Boolean DIFFE-
RENCEs.



$u/0 - ?$
 $u/1 - ?$


FOR DETECTION OF U/D \Leftrightarrow

1) $u(x_0, x_1, \dots, x_{m-1}) = 1$ CONTROL.

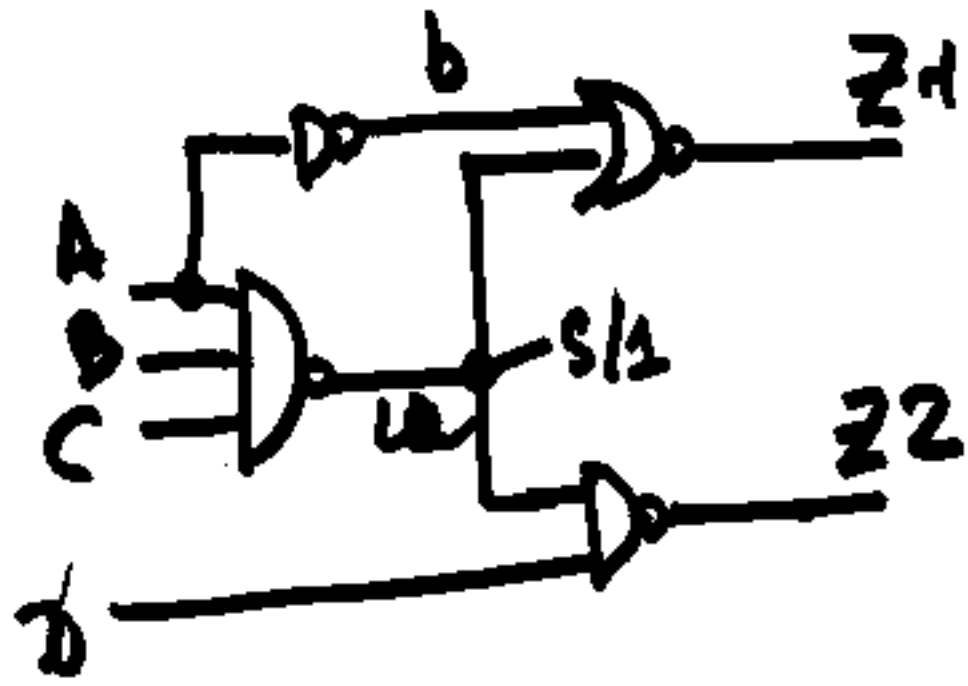2) $\frac{\partial z_1}{\partial u} = 1$ or $\frac{\partial z_2}{\partial u} = 1 \dots$ or $\frac{\partial z_k}{\partial u} = 1$

THUS

$$u(x_0, x_1, \dots, x_m), \begin{matrix} \text{CONTROL} \\ \left(\frac{\partial z_1}{\partial u} \right. \\ \left. \frac{\partial z_2}{\partial u} \right) \end{matrix} \vee \begin{matrix} \text{OBSERVE} \\ \left(\frac{\partial z_1}{\partial u} \right. \\ \left. \frac{\partial z_2}{\partial u} \right) \vee \dots \end{matrix}$$
$$\vee \left(\frac{\partial z_k}{\partial u} \right) = 1$$



u/1-?

CONTROLLABILITY

u=0 =>

$$u = \overline{ABC} = 0$$

$$ABC = 1 \Rightarrow A=1, B=1, C=1$$

observability

$$\frac{\partial z_1}{\partial u} = (\overline{0 \vee b}) \oplus (\overline{1 \vee b}) = \overline{b} \oplus \overline{b} = \overline{b}$$

$$\frac{\partial Z_2}{\partial u} = (\overline{0 \cdot D}) \oplus (\overline{1 \cdot D}) = 1 \oplus \overline{D} = D.$$

$$u(A, B, C) \cdot \left(\frac{\partial Z_1}{\partial u} \vee \frac{\partial Z_2}{\partial u} \right) =$$

$$= ABC (\overline{b} \vee D) = ABC(A \vee B) =$$

$$= ABC \vee ABCD = ABC$$

TEST

ABCD
1111#.

Faults at
line u are undetectable
(cannot observe distortion of a
signal at u) \Leftrightarrow

$$\text{any } i \quad \frac{\partial z_i}{\partial u} \equiv 0$$