

# Gate - Level Fault Masking

8

## Interwoven Logic

COMBINATION OF VOTING AND COMPUTING

Critical faults  $\Rightarrow$  force a certain gate output

Subcritical faults  $\Rightarrow$  do not force a gate output

Gate	Critical Faults	Subcritical Faults
AND	$1 \rightarrow 0$	$0 \rightarrow 1$
OR	$0 \rightarrow 1$	$1 \rightarrow 0$
NOT	$0 \rightarrow 1, 1 \rightarrow 0$	None
NAND	$1 \rightarrow 0$	$0 \rightarrow 1$
NOR	$0 \rightarrow 1$	$1 \rightarrow 0$
XOR	None	$0 \rightarrow 1, 1 \rightarrow 0$

Interwoven Logic: critical faults at one layer result in output errors which are subcritical input faults for the following layer

Any fault is stopped within two layers

ALL-NAND networks or alternating layers of AND and OR gates

Very high redundancy


INTERWOVE LOGIC: NAND NETWORKS

EVERY BIT  $x$  replaced by  $(x_1, x_2, x_3, x_4)$

EVEN LAYERS: GROUPING:  $\{x_1, x_4\}, \{x_2, x_3\}$

ODD LAYERS GROUPING:  $\{x_1, x_2\}, \{x_3, x_4\}$

Example

 

Original Non redundant device

$$x \Rightarrow (x_1, x_2, x_3, x_4)$$


$$y \Rightarrow (y_1, y_2, y_3, y_4)$$

$$z \Rightarrow (z_1, z_2, z_3, z_4)$$

$$w \Rightarrow (w_1, w_2, w_3, w_4)$$

quadded logic

Redundancy  $R=4$ .

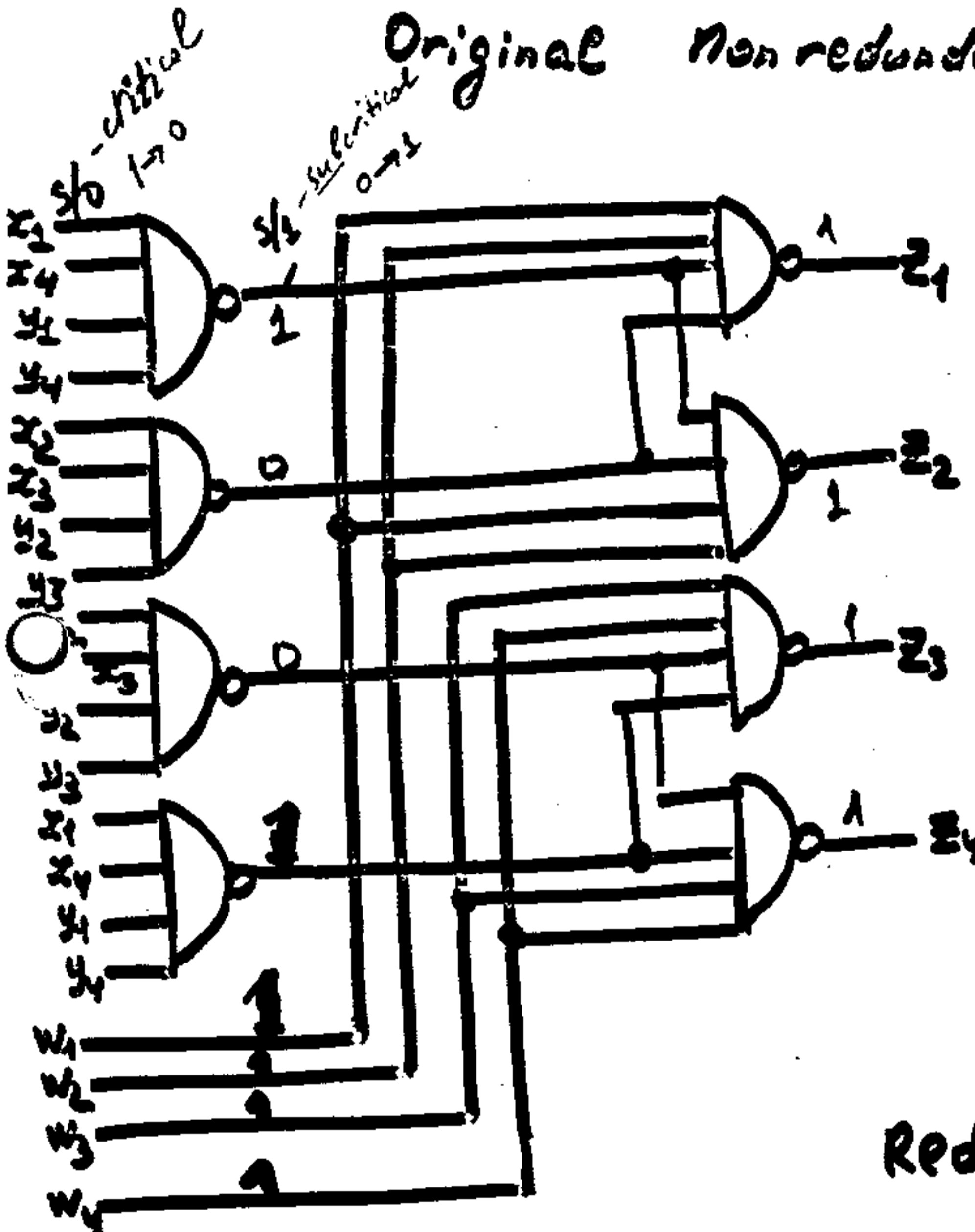

Redundant Fault-Tolerant device  
 with self-error-correcting of single  
 errors

# Interwoven Logic

To correct  $t$  errors:

1. Redundancy  $R = (t+1)^2$  in a number of gates  
( $t=1 \Rightarrow R=4$ )
2. Every gate has  $(t+1)$  times more inputs than the corresponding gate in the original device

Very expensive!

(D. P. Sarnorek, R. S. Swartz, "The Theory and Practice of Reliable System Design: Digital Press, 1982, Ch 3)