

Detection of Single Errors.

Parity Checking.

$$d(U) = 2$$

One equation ($r = 1$) : $(v_1, \dots, v_n) \in U$ if $v_1 \oplus v_2 \oplus \dots \oplus v_n = 0$

$$k = n - 1$$

Detects all errors of *odd* multiplicities used for memories and busses.

Example :


$$n = 4, k = 3$$

v_1	v_2	v_3	v_4
0	0	0	0
0	0	1	1
0	1	0	1
0	1	1	0
1	0	0	1
1	0	1	0
1	1	0	0
1	1	1	1

← parity (check) bit

LECTURE 9 8/2/53

MEMORY WITH PARITY CHECKING ²²₆₅

 


PARITY PREDICTION FOR PLAS

2166

EXAMPLE $m=3$ $k=7$ $r=1$

NUMBER	f_0	f_1	f_2	f_3	f_4	f_5	f_6	f_7	CHECK
0	0	0	1	1	1	1	1	1	
1	1	0	1	0	0	1	0	1	
2	1	0	1	0	1	1	1	1	
3	0	0	1	1	0	0	0	0	
4	1	0	0	0	1	0	0	0	
5	0	1	1	1	0	0	0	1	
6	0	0	0	0	0	1	0	1	
7	0	0	0	0	1	0	1	0	

 

Self - Error Detection Based on Parity Prediction.

Example : *Binary Adder.*

$$s = a + b$$

$$a = (a_{k-1}, \dots, a_0, a_c)$$

$$b = (b_{k-1}, \dots, b_0, b_c)$$

$$s = (s_{k-1}, \dots, s_0, s_c)$$

a_c, b_c, s_c - check bits.

$$a_c = \bigoplus_{i=0}^{k-1} a_i$$

$$b_c = \bigoplus_{i=0}^{k-1} b_i$$

$$s_c = \bigoplus_{i=0}^{k-1} s_i$$

Let c_i ($i = 1, \dots, k-1$) is the carry from ($i - 1$)th bit.


Then

$$s_c = \bigoplus_{i=0}^{k-1} s_i = \bigoplus_{i=0}^{k-1} a_i \oplus \bigoplus_{i=0}^{k-1} b_i \oplus \bigoplus_{i=0}^{k-1} c_i = a_c \oplus b_c \oplus \bigoplus_{i=0}^{k-1} c_i$$

In the next fig. carry circuits are *duplicated* to avoid propagation of errors.

D. K. Pradhan "Fault Tolerant Computing"
vol 1, ch 5, Prentice Hall.

EXAMPLE $m=3$

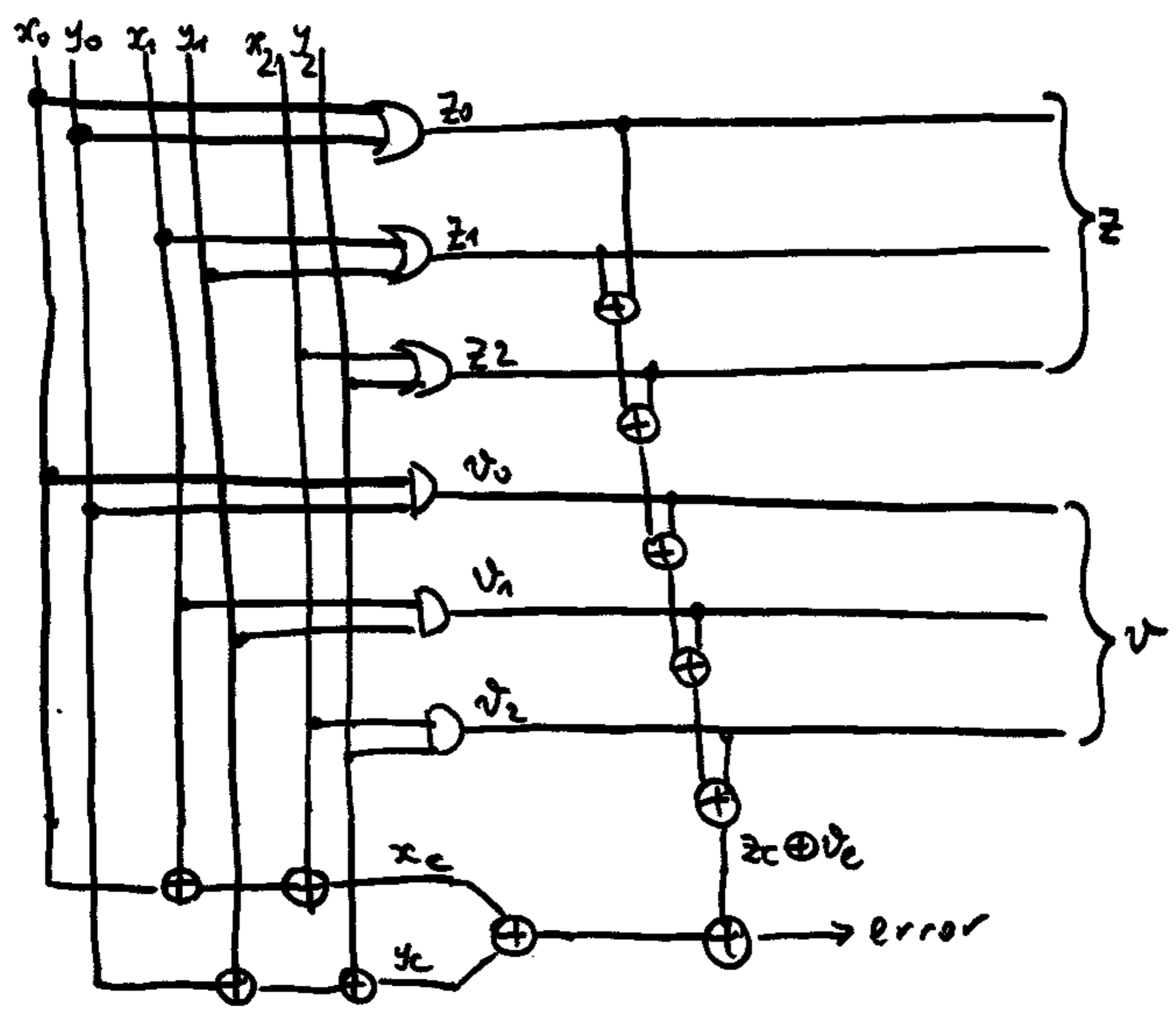

Any single error in $(z_0, z_1, z_2, v_0, v_1, v_2)$ is detected
output

Any single error in $(x_0, y_0, x_1, y_1, x_2, y_2)$ is detected
INPUT

Since x_i is involved in computing three parity bits z_c, v_c and x_c
 (y_i is involved in z_c, v_c , any y_c)